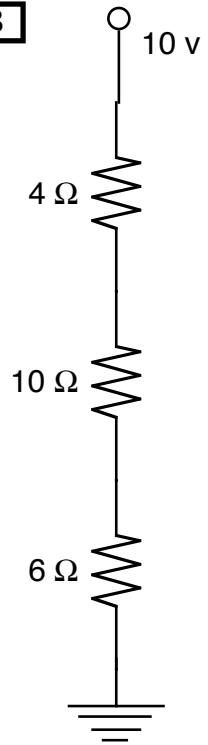





# Electrical Circuits

## Equivalent Resistance for a Series Circuit


**3**




**4**

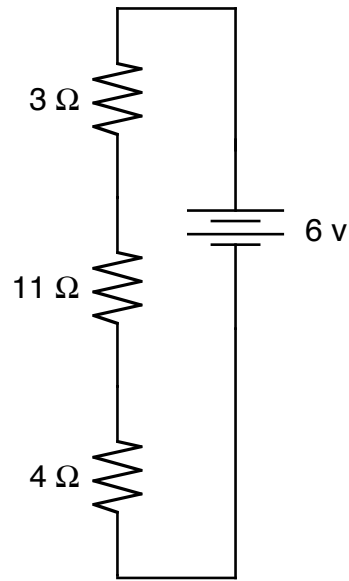


**5**

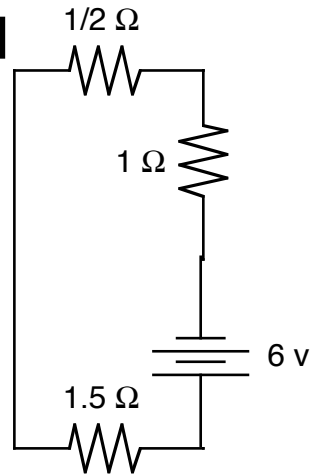

**6**





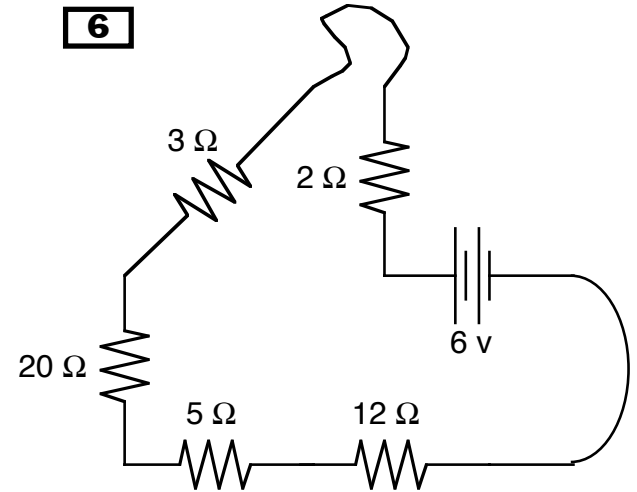


**7**

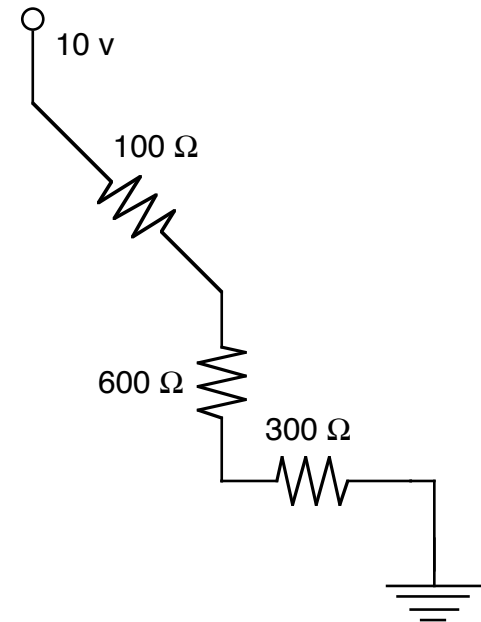


# Electrical Circuits
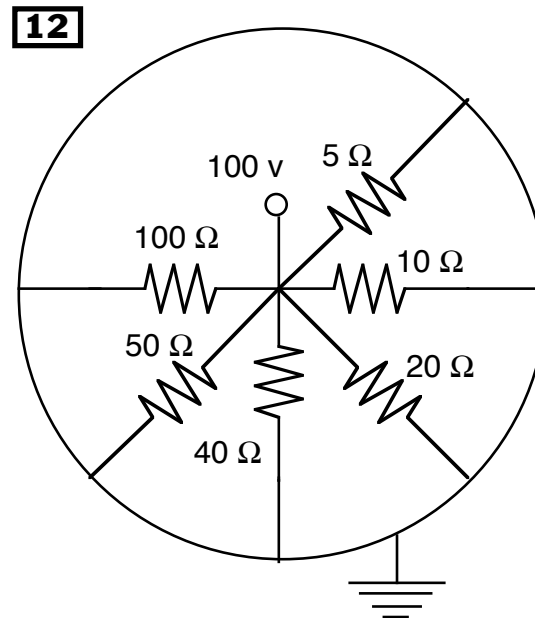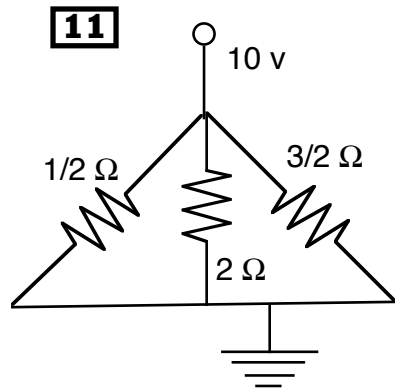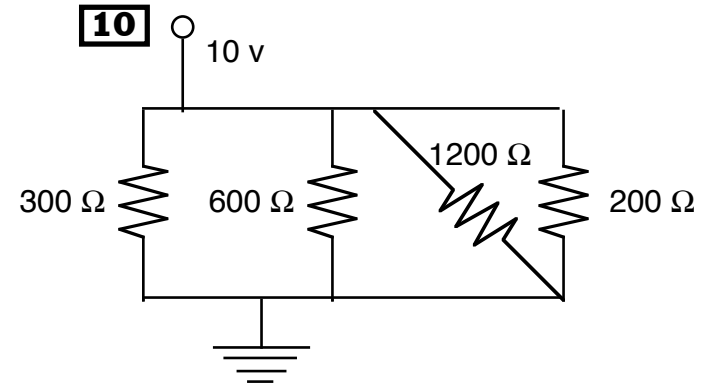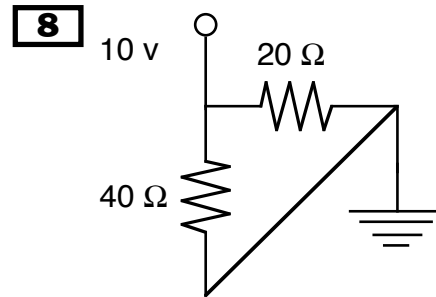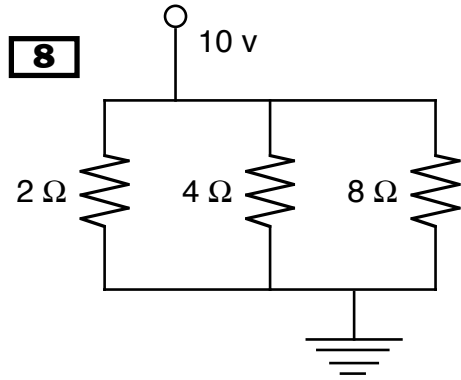
## Equivalent Resistance for a Parallel Circuit




## Electrical Circuits

13

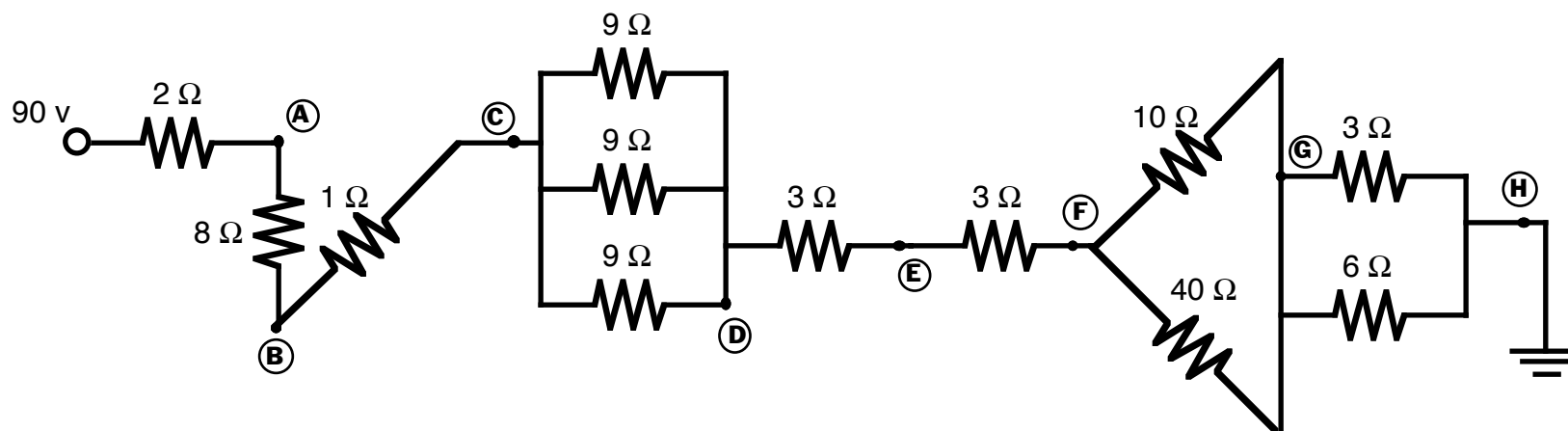


## Electrical Circuits


**14**

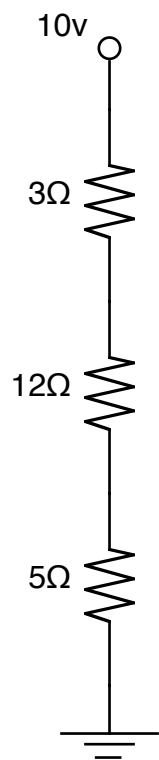

**15**

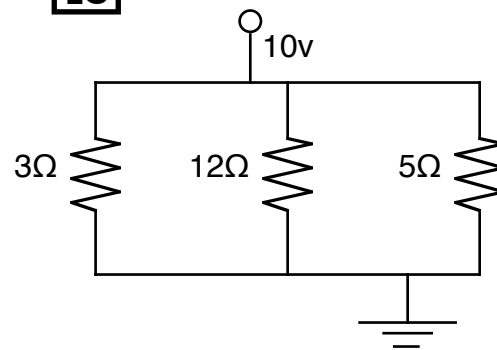


**16**

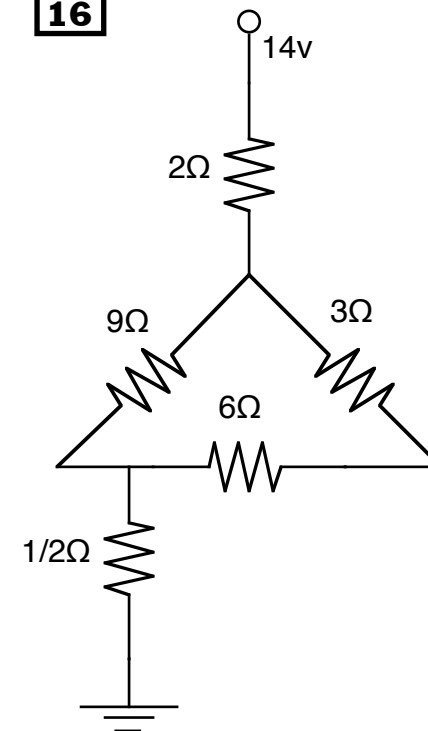

## Electrical Circuits


---

**17**

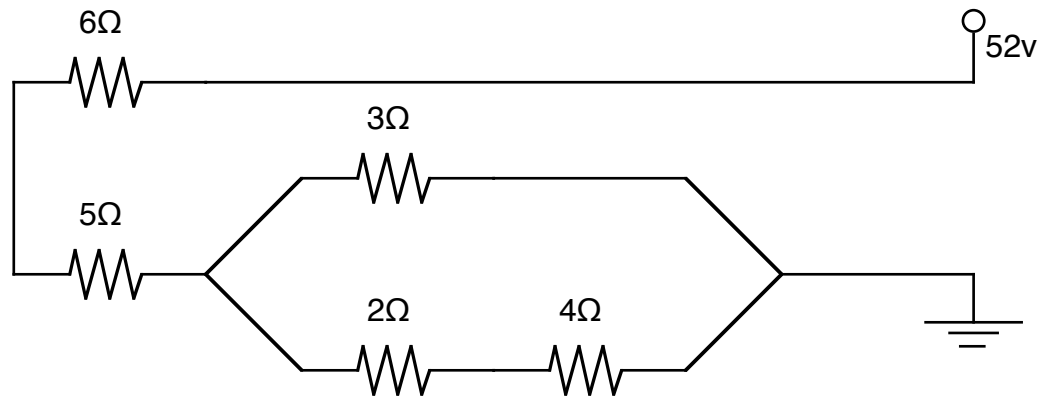

## Electrical Circuits


18

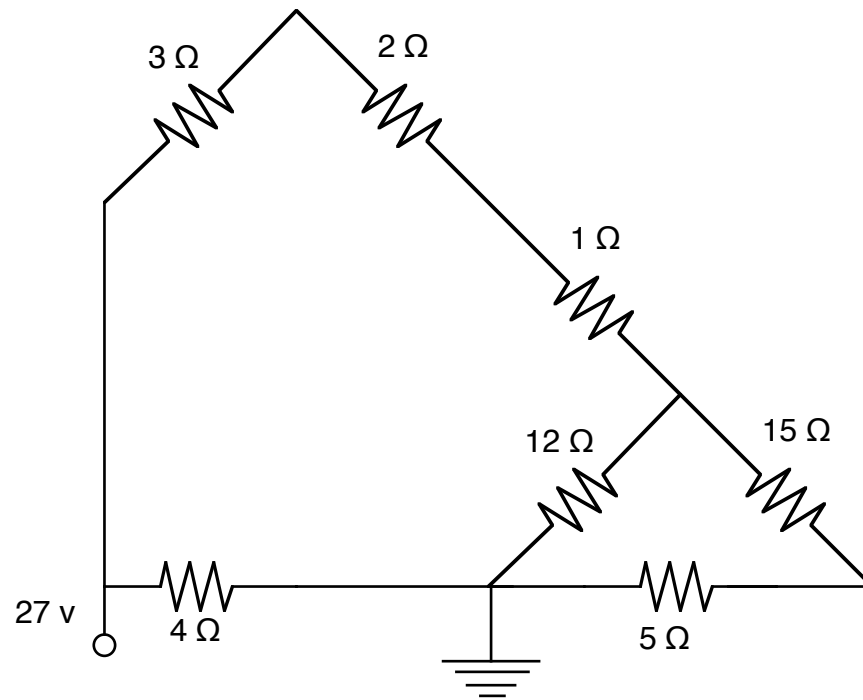

## Electrical Circuits

---


**19**

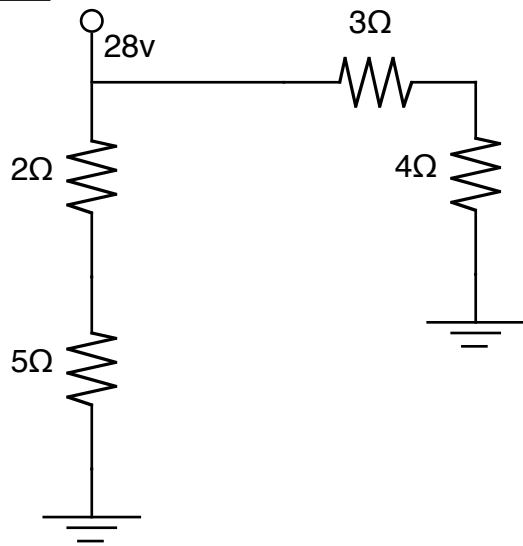

## Electrical Circuits

---


**20**

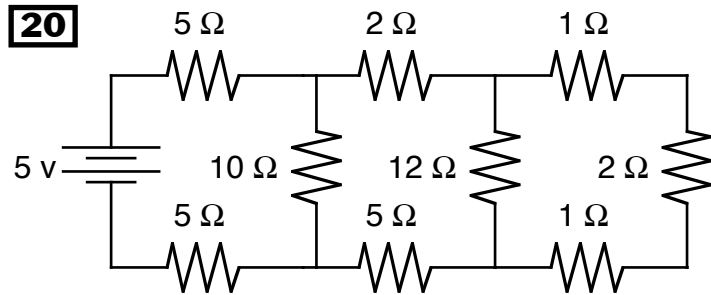

## Electrical Circuits

---


**21**

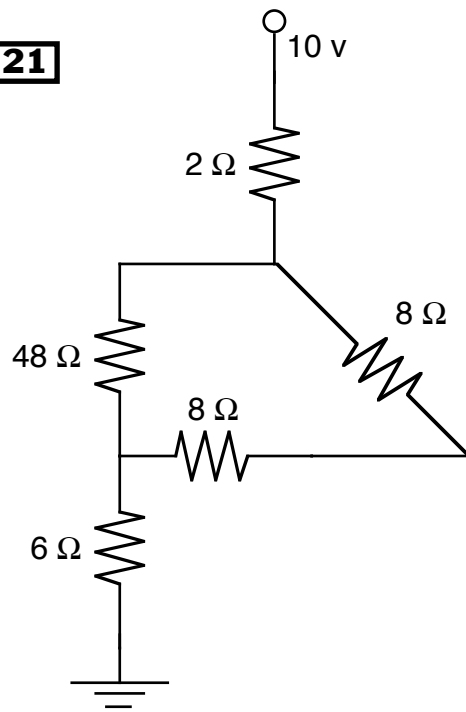

## Electrical Circuits


---

**22**

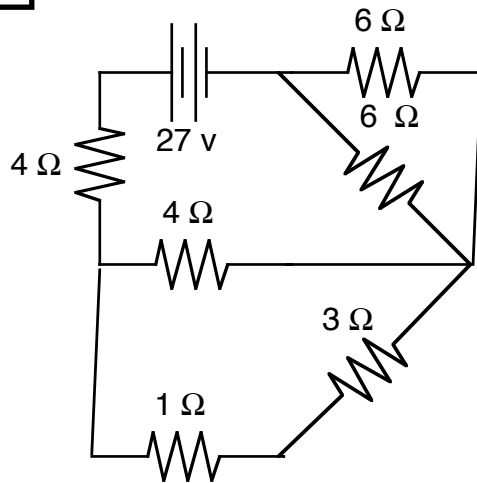

## Electrical Circuits

**23**


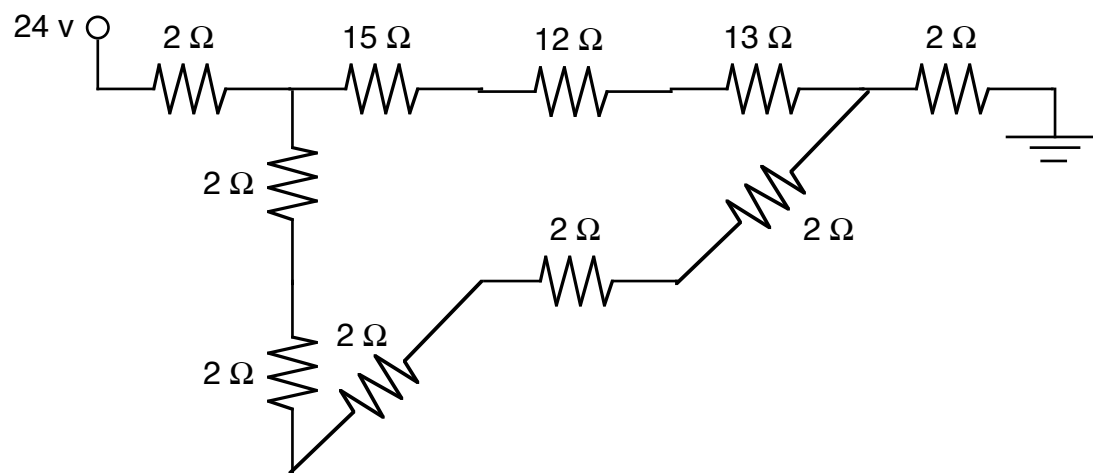


## Electrical Circuits

Calculate the circuit's total resistance

Find the voltage drop across and current through each original resistor

Find the voltage's  $V_1$  and  $V_2$ .

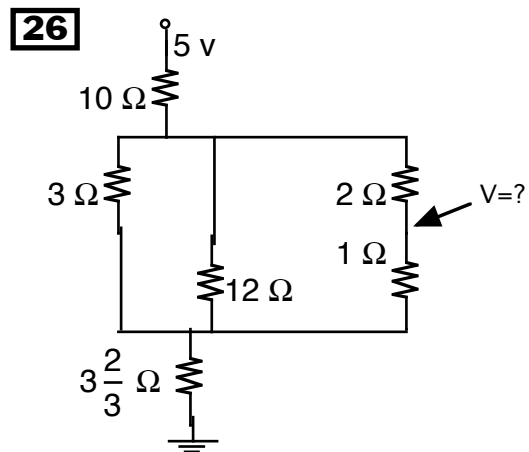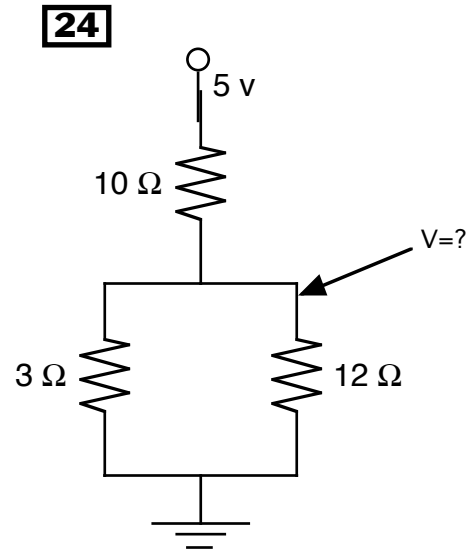


## Electrical Circuits

---

Calculate the circuit's total resistance

Find the voltage drop across and current through each original resistor


Find the voltage's  $V_1$  and  $V_2$ .

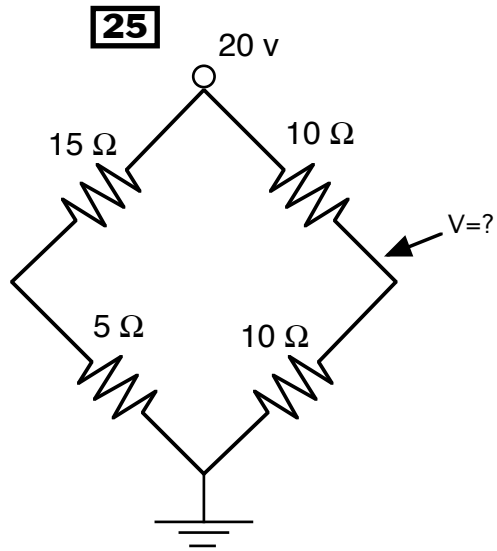
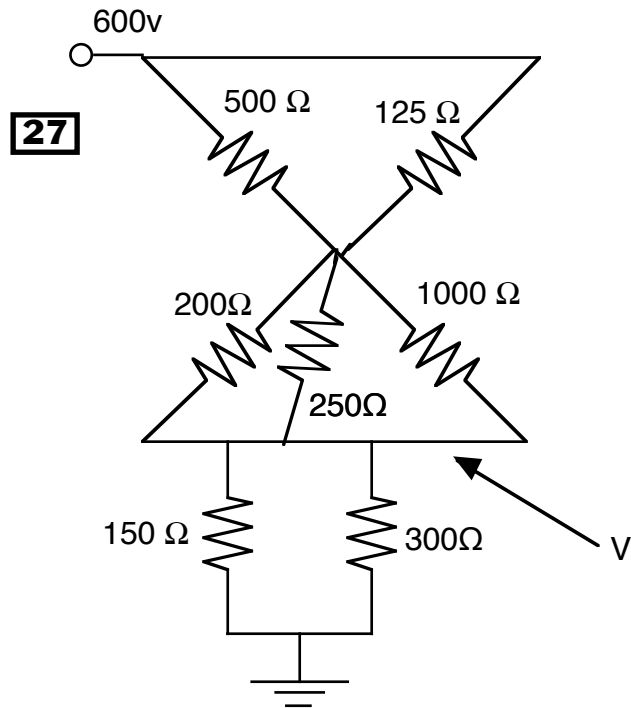
## Electrical Circuits

---


- Calculate the circuit's total resistance  
Find the voltage drop across and current through each original resistor  
Find the voltage's  $V_1$  and  $V_2$ .  
Find the power dissipated by each resistor.



## Electrical Circuits

Calculate the circuit's total resistance  
Find the voltage drop across and current through each original resistor  
Find the voltage's  $V_1$  and  $V_2$ .


**28**

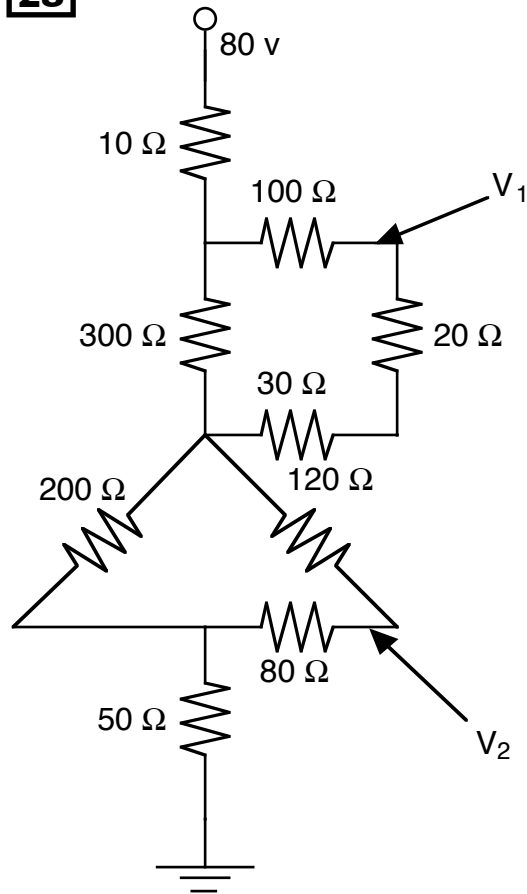

## Electrical Circuits

---

**29**

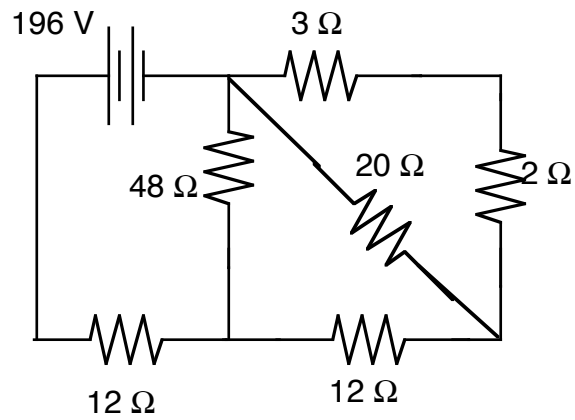

## Electrical Circuits

---

**30**

